

**Microcontroller Applications
Department of Instrumentation
Engineering**

Analogue (ADC & DAC) Interfacing

In this Lecture

Interface 8051 with the following Input/Output Devices

- Transducer/Sensors
- Analogue-to-Digital Conversion (ADC)
- Digital-to-Analogue Conversion (DAC)

Analog-to-digital converter (ADC)

- ◆ ADC convert analogue voltage to digital numbers so that microcontrollers can handle and process the data.
- ◆ Used for data acquisition
- ◆ **n-bit resolution**, where $n = 8, 12, 16$ or even 24 bits.
- ◆ **Higher**-resolution ADC provides a **smaller step size**.
- ◆ **Step size is the smallest change** that can be recognized by ADC.

Analog-to-digital converter (ADC)

- An ADC has a resolution of 8 bits, the range is divided into $2^8=256$ steps (from 0 – 255). But there are 255 quantization levels.


$$\text{Step Size} = \frac{V_{cc}}{2^n}$$

- V_{cc} is the reference voltage of ADC with **n-bit resolution**

Table 10.3 : Resolution versus Step Size for ADC (if $V_{cc} = 5V$)

<u>n-bit</u>	<u>Number of steps</u>	<u>Step Size (mV)</u>
8	$2^8 = 256$	$5/256 = 19.53$
10	$2^{10} = 1024$	$5/1024 = 4.88$
12	$2^{12} = 4096$	$5/4096 = 1.2$
16	$2^{16} = 65536$	$5/65536 = 0.076$

ADC0804 Chip (Free Running Mode)

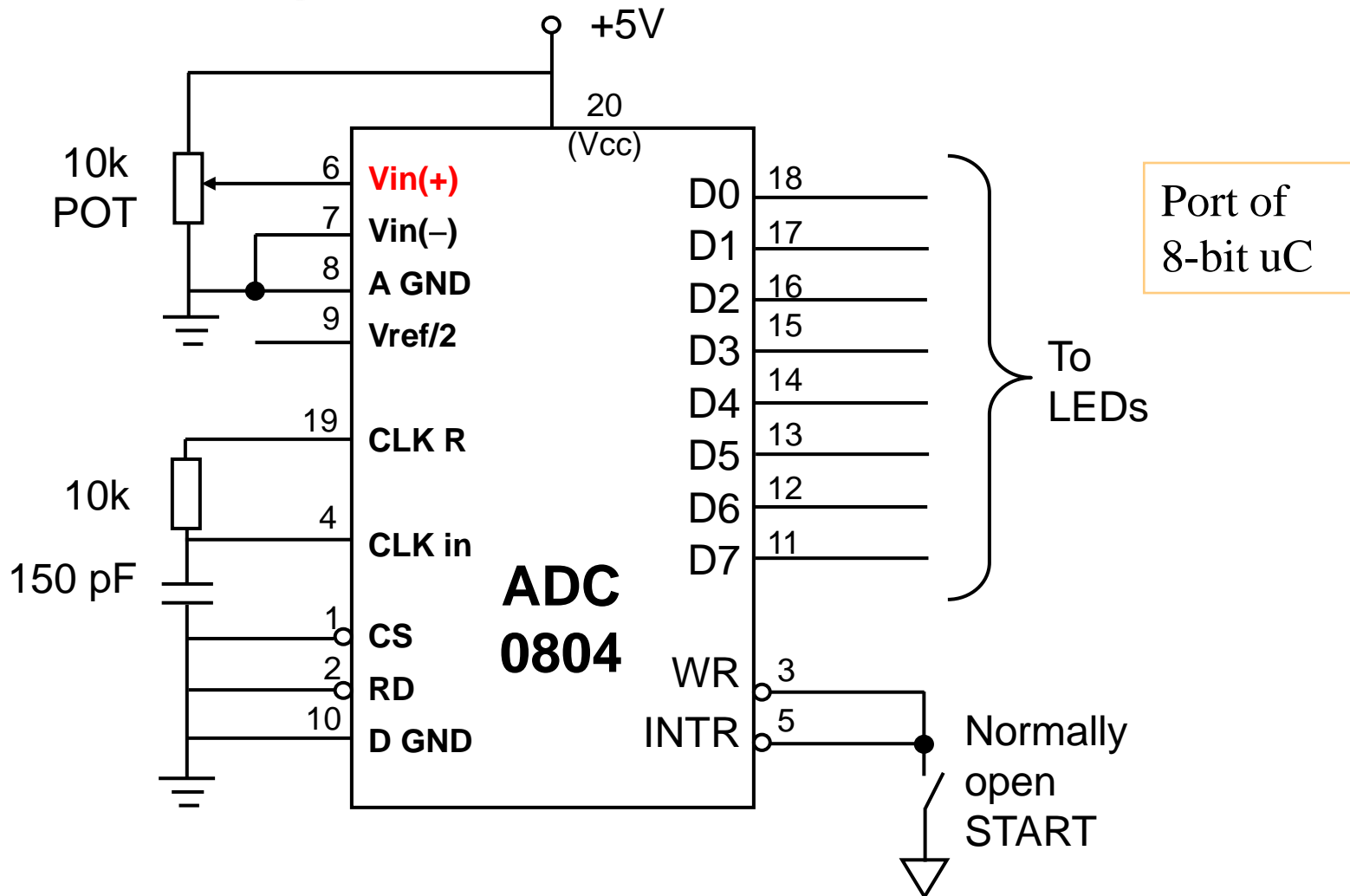

ADC0804 Chip

V_{CC}

This is the +5V power supply. It is also used as a reference voltage when the Vref/2 (pin 9) input is **open**.

$$\text{step size} = \frac{2 \times \frac{V_{REF}}{2}}{2^8} = \frac{V_{REF}}{256}$$

Vref/2

Input voltage pin used for the reference voltage. If this pin is **open**, the analog input voltage for the the ADC is ranged from 0 to 5 volts.

ADC0804 has
resolution of
8 bits

Vref/2 (V)	Vin (V)	Step Size (mV)
Not connected	0 to 5	5/256 = 19.53
2.0	0 to 4	4/256 = 15.62
1.5	0 to 3	3/256 = 11.71
1.28	0 to 2.56	2.56/256 = 10
1.0	0 to 2	2/256 = 7.81
0.5	0 to 1	1/256 = 3.90

Pin Vref/2 is open, Step size = 19.53 mV

ADC0804 Chip

D0 – D7

D0 – D7 are the digital data output pins. These are the tri-state buffered and the converted data is accessed only when CS = 0 and RD is forced low. The output voltage:

$$D_{\text{out}} = \frac{V_{\text{in}}}{\text{Step size}}$$

Analog Ground and Digital Ground


Analog ground is connected to the ground of the analog signal while digital ground is connected to the ground of the Vcc pin.

Question: An analog input voltage of 3.5V, Pin Vref/2 is open.

Solution:

$D_{\text{out}} = 3.5\text{V} / 19.53 \text{ mV} = 179$ (depends on accuracy of ADC)

Testing the ADC0804

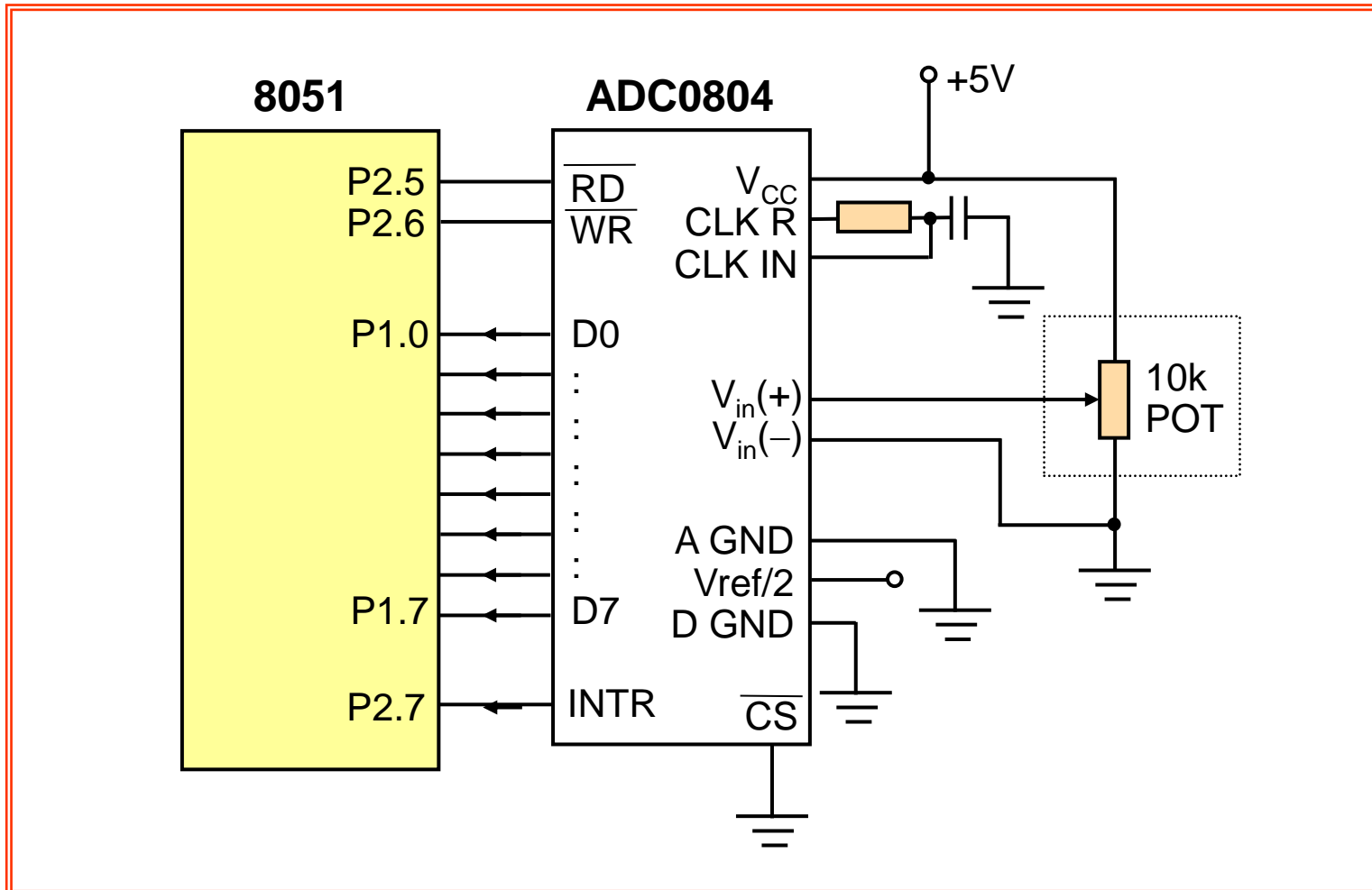


Example of ADC Application

- ◆ Temperature detection
- ◆ A temperature sensor (LM34 or LM35) is interfaced to the 8051 via an ADC (ADC0804)
- ◆ The output voltage from the LM34/LM35 is linearly proportional to the measuring temperature
- ◆ The ADC0804 converts the output voltages from the LM34/LM35 into digital signals, which correspond to the measured temperature.


Features of ADC 0808

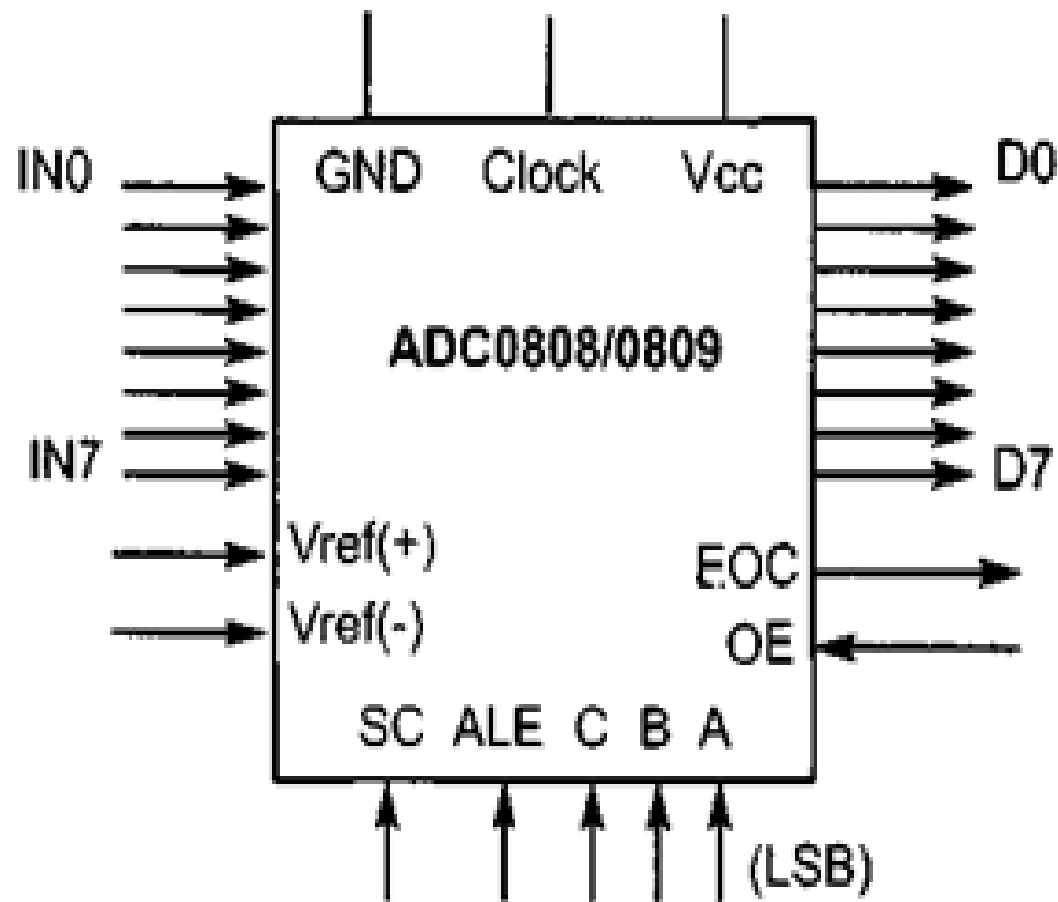1. Inbuilt 8 analog channels with multiplexer.
2. Zero or full scale adjustment is not required.
3. 0 to 5 V input voltage range with a single polarity 5 V supply.
4. Output is TTL compatible.
5. High speed.
6. Low conversion time(100 μ s).
7. High accuracy.
8. 8-bit resolution.
9. Low power consumption (less than 15 mW).
10. Easy to interface with all microcontroller.
11. Minimum temperature dependence.



ADC0808/0809 ANALOG CHANNEL SELECTION

Analog Channel	ADDRESS LINES		
	C	B	A
IN0	0	0	0
IN1	0	0	1
IN2	0	1	0
IN3	0	1	1
IN4	1	0	0
IN5	1	0	1
IN6	1	1	0
IN7	1	1	1

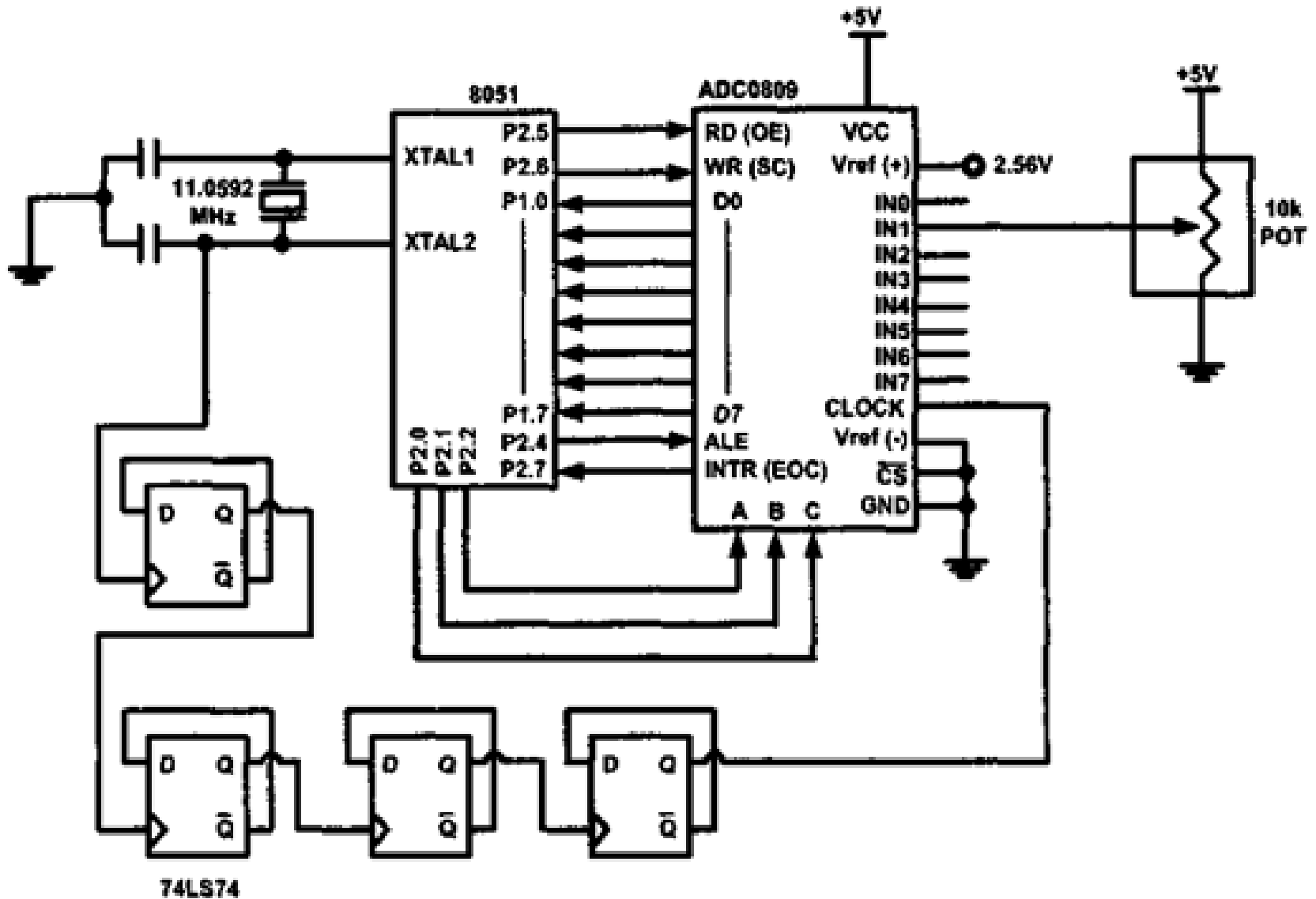



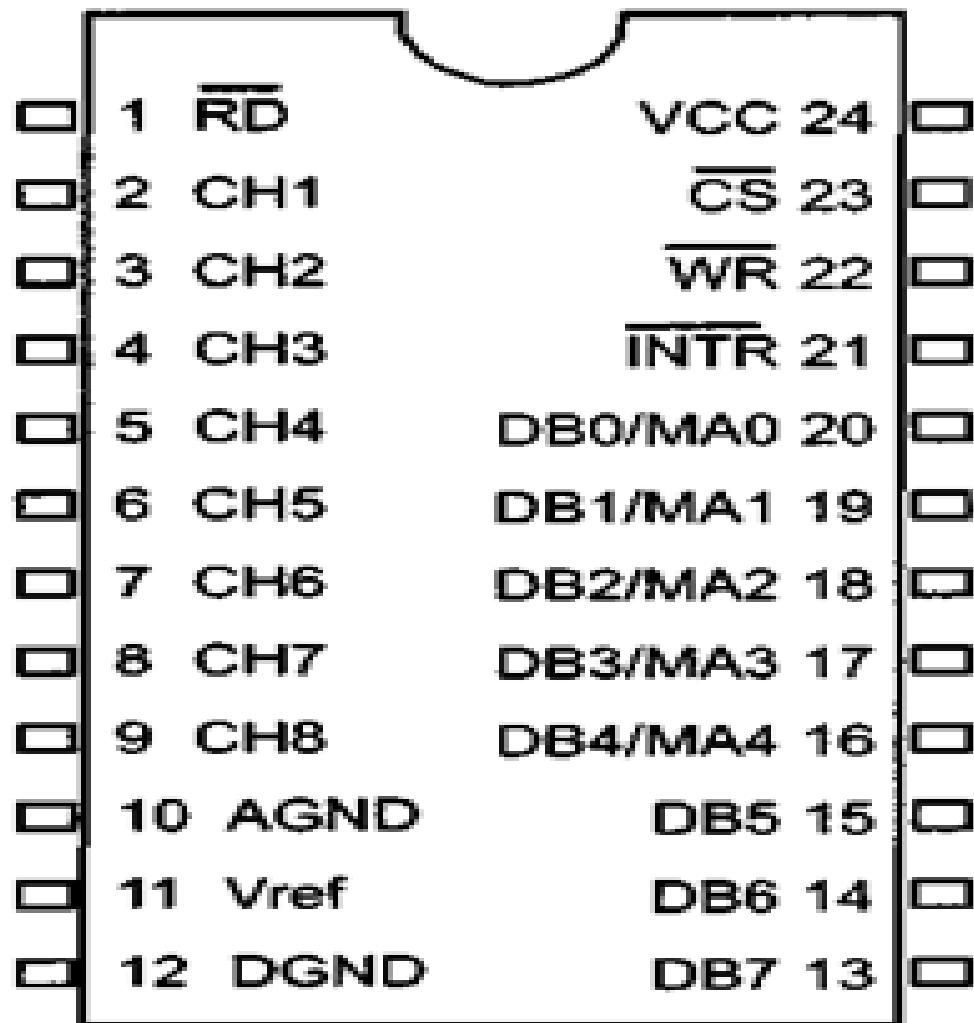


Figure 13-8. ADC0848 Chip

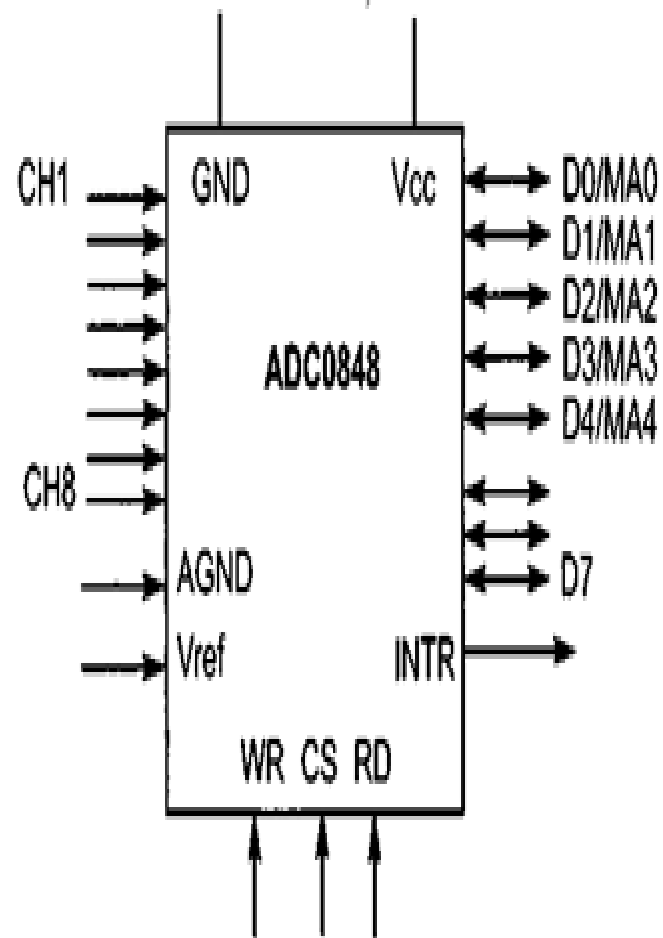

Selected Analog Channel	MA4	MA3	MA2	MA1	MA0
CH1	0	1	0	0	0
CH2	0	1	0	0	1
CH3	0	1	0	1	0
CH4	0	1	0	1	1
CH5	0	1	1	0	0
CH6	0	1	1	0	1
CH7	0	1	1	1	0
CH8	0	1	1	1	1

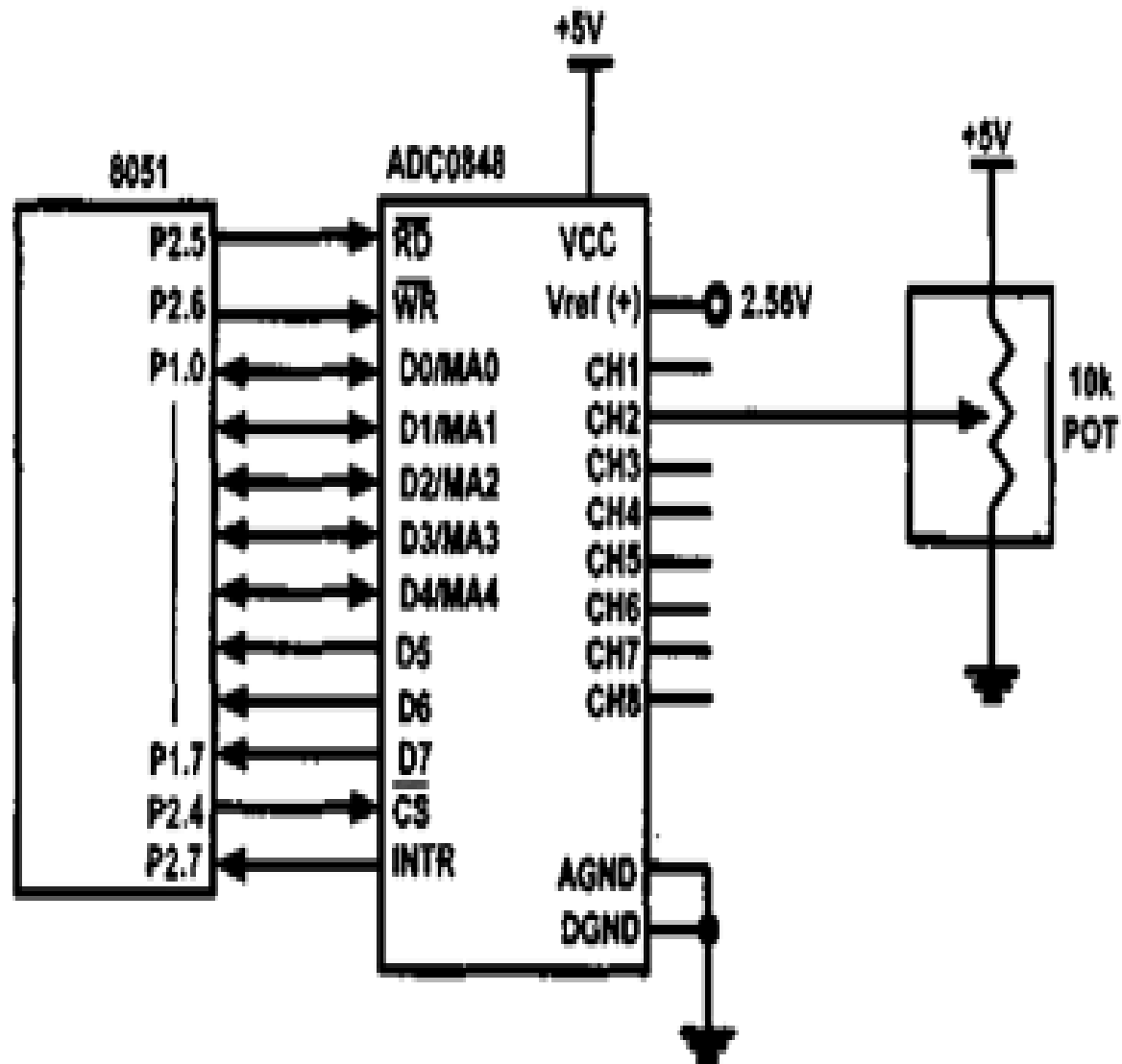

Serial ADC chips

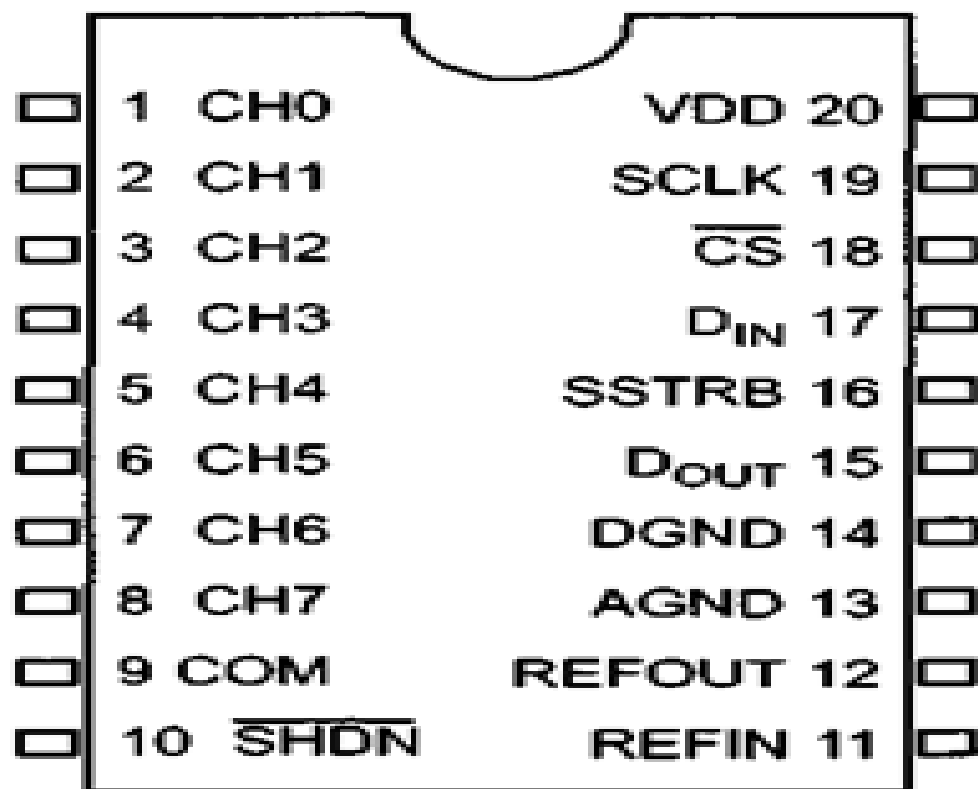


Figure 13-12. MAX1112 Chip

Digital-to-Analog (DAC) Conversion

- ◆ The digital-to-analog converter (DAC) is a device widely used to convert digital values to analog signals.
- ◆ It does the reverse operation of an ADC
- ◆ The resolution of DAC depends on the no. of binary bits input to it.
- ◆ The common ones are 8, 10 and 12 bits.
- ◆ An 8-input DAC provides 256 discrete voltages (or current) levels of output. (The 12-bit DAC gives 4096 discrete levels).


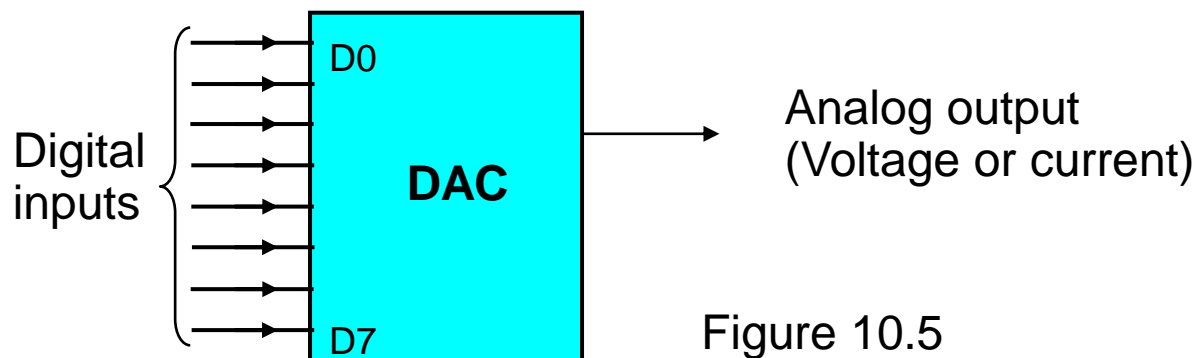


Figure 10.5

DAC0808 Chip (MC1408)

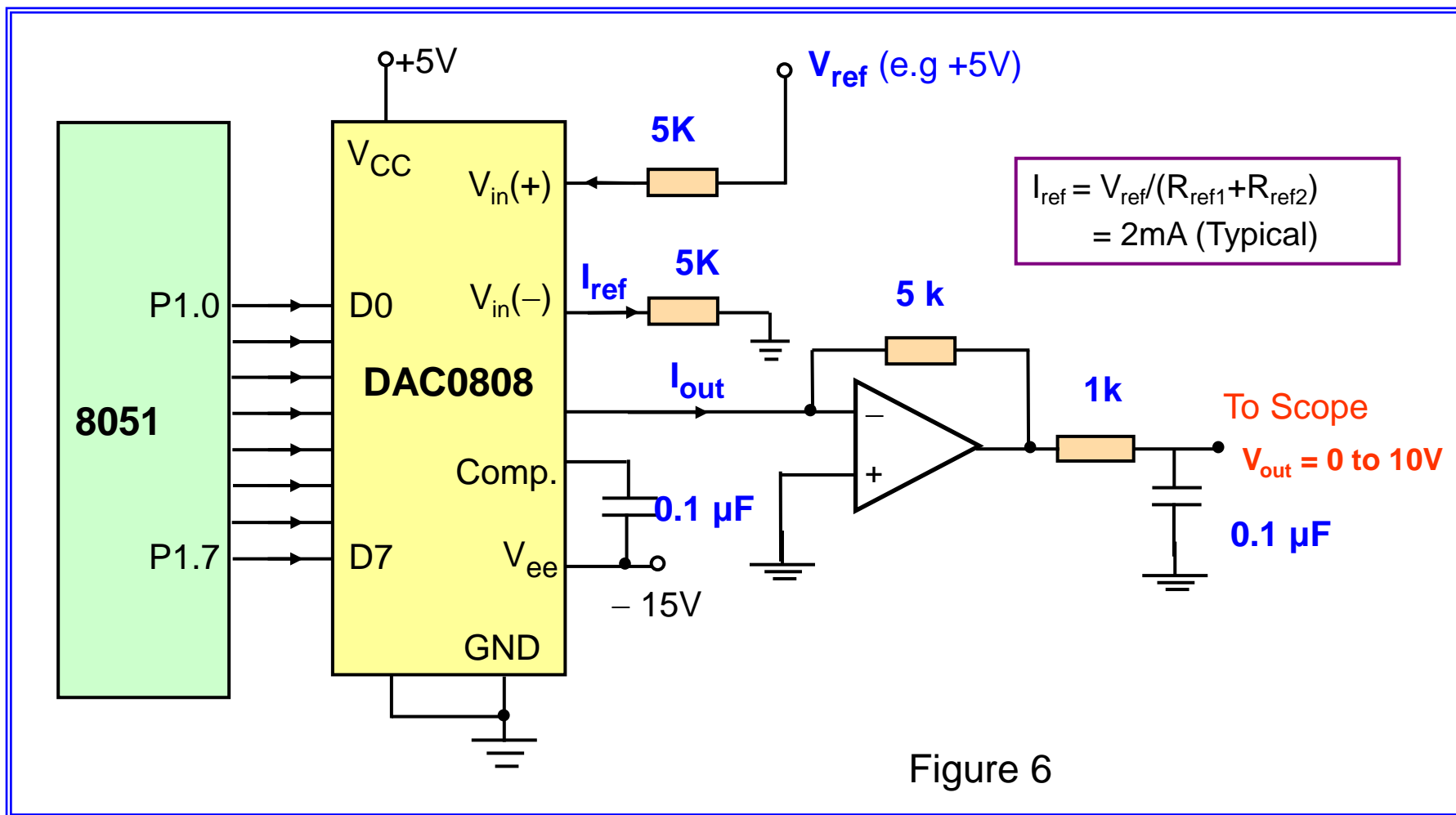

DAC0808 Chip (MC1408)

Operating Principle

- In the DAC0808, the digital inputs are converted to corresponding current (I_{out}).
- Then by connecting a resistor to the I_{out} pin, the current will further convert to voltage level.
- The total current provided by the output I_{out} pin is a function of the reference current (I_{ref}) and is follows:

$$I_{out} = I_{ref} \left(\frac{D_7}{2} + \frac{D_6}{4} + \frac{D_5}{8} + \frac{D_4}{16} + \frac{D_3}{32} + \frac{D_2}{64} + \frac{D_1}{128} + \frac{D_0}{256} \right)$$

Converting I_{out} to voltage (V_{out})

Connect the output pin I_{out} to a output standard resistor and hence convert this current to a voltage.

$$\text{Output voltage, } V_{out} = I_{out} \times R_o$$

Example 3

Assume that $R_o = 5k\Omega$, $R_{ref1} = 1k\Omega$, $R_{ref2} = 1.5k\Omega$ and using a standard 5V supply connected to $V_{ref(+)}$, calculate V_{out} for the following binary inputs.

(a) 1001 1001 (99H)

(b) 1100 1000 (C8H)

Solution:

$$I_{ref} = \frac{5}{1000 + 1500} = 2mA$$

(a) 99H = 153_{10}

$$I_{out} = (2mA) \frac{153}{256} = 1.195mA$$

$$V_{out} = (1.195mA)(5000k\Omega) = 5.975V$$

(b) C8H = 200_{10}

$$I_{out} = (2mA) \frac{200}{256} = 1.562mA$$

$$V_{out} = (1.562mA)(5000k\Omega) = 7.8125V$$

Example 4

In order to generate a stair-step ramp, set up the circuit as in Figure 6 and connect the output to an oscilloscope. Then write a program to send data to the DAC at port 1 to generate a stair-step ramp.

Solution:

```
                ORG 0H
                CLR    A
AGAIN:          MOV    P1, A    ; send data to DAC
                INC    A        ; count from 0 to FFH
                ACALL  DELAY    ; let DAC work and recover
                SJMP   AGAIN
                END
```

Example 5

Use the circuit in Figure 6, write a program to generate a sine wave of full-scale 10V output. If the output is connected to a CRO, draw the display on the CRO screen.

Solution:

Assume 10V full-scale voltage for the DAC output.

$$V_{\text{out}} = [5 + (5 \sin \theta)] \text{ V}$$

A table is drawn up to list the magnitude of the sine of angles between 0 and 360 degrees. The table values are integer numbers representing the voltage magnitude for the sine θ .

Table 10.5 gives the angles, the sine values, the voltage magnitudes and the integer values representing the voltage magnitude for each angle (with 30° interval).

$V_{out} \times 256/10$

Table 5 Angle vs Voltage Magnitude for Sine Wave

Angle θ (degree)	Sine θ	Vout $5V + (5\sin \theta)$	Voltage Values sent to DAC
0	0	5	128
30	0.5	7.5	192
60	0.866	9.33	238
90	1.0	10	255
120	0.866	9.33	238
150	0.5	7.5	192
180	0	5	128
210	-0.5	2.5	64
240	-0.866	0.669	17
270	-1.0	0	0
300	-0.866	0.669	17
330	-0.5	2.5	64
360	0	5	128

256 steps and full scale Vout is 10 volts

$9.33 \times 256/10$

Program Generating a Sine Wave


```

                ORG 0H
AGAIN:         MOV     DPTR, #TABLE
                MOV     R2, #COUNT
BACK:         CLR     A
                MOVC    A, @A+DPTR
                MOV     P1, A
                INC     DPTR
                DJNZ    R2, BACK
                SJMP    AGAIN
                ;
                ORG     300
TABLE:        DB     128, 192, 238, 255, 238, 192
                DB     128, 64, 17, 0, 17, 64, 128
                ;

```

; To get a better looking sine wave, regenerate the look-up table for 2-degree angles
 END

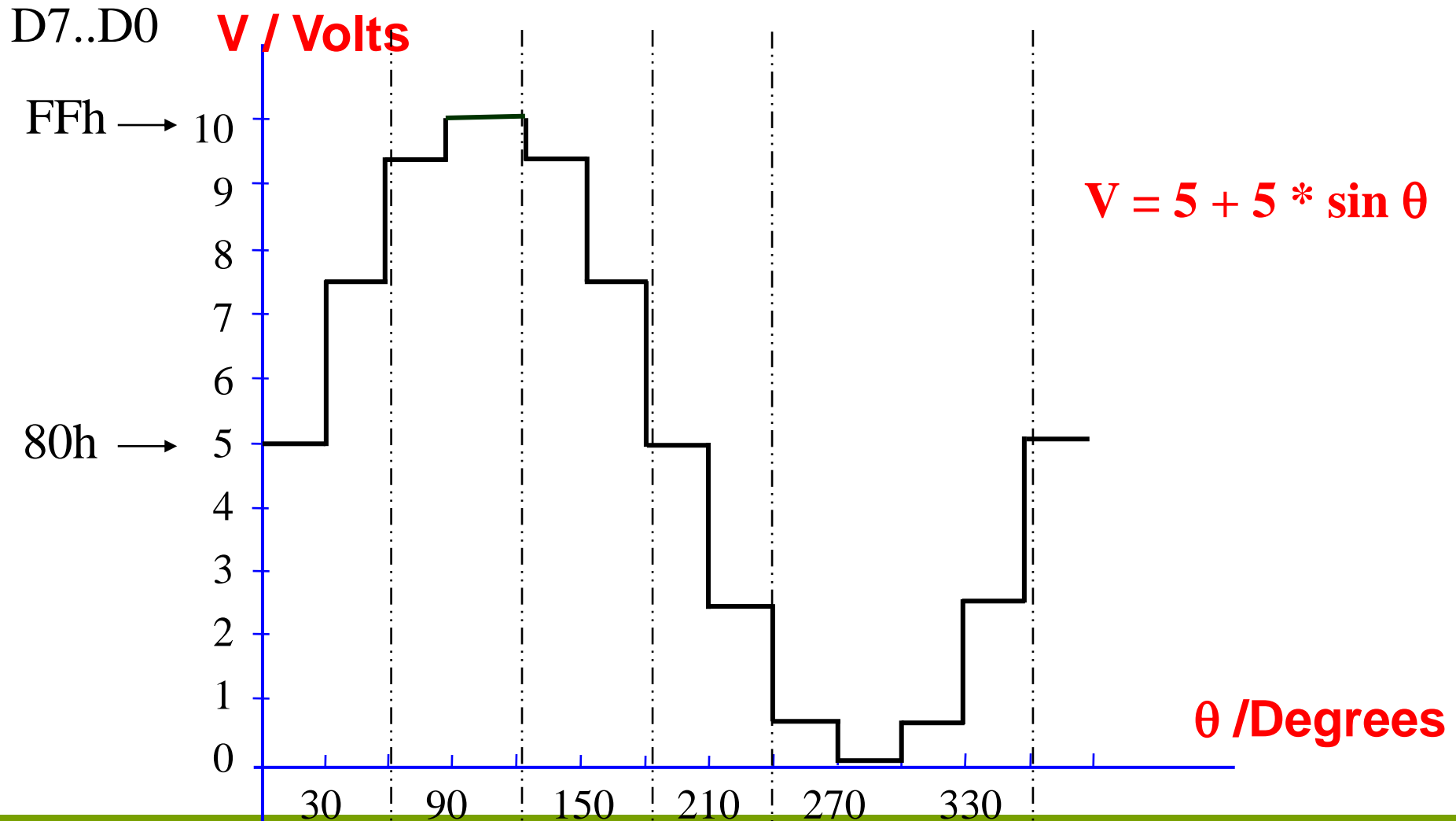Display on the Generating Sine Wave on CRO



Transducer/sensors

- ◆ Digital computer/microcontrollers use binary values, but in the physical world most things is in analog nature (continuous).
- ◆ Data (such as temperature, pressure, humidity, velocity, voltage) are analog data.
- ◆ A device called **transducer** is used to convert the physical quantity to electrical signals (i.e. voltage, current).
- ◆ Transducer are also referred to as **sensors**.
- ◆ Sensors for temperature, velocity, pressure, light, and many other natural quantities can produce an output voltage (or current) which the value is proportional to the quantity being measured.
- ◆ Then an analog-to-digital converter is used to **translate the analog voltage to digital numbers** so that microcontroller can read and process them.

Temperature sensors (Thermistor)

- ◆ Temperature can be converted to electrical signals by thermistor.
- ◆ Thermistor is a **kind of resistor** responds to temperature change by changing its resistance.
- ◆ But its response is **not linear**, as seen in the Table 10.1 below.

Table 10.1

Temperature (°C)	Thermistor Resistance (kΩ)
0	29.490
25	10.000
50	3.893
75	1.700
100	0.817

Temperature sensors (LM34 and LM35)

- **LM34** series are precision integrated-circuit temperature sensors whose output voltage is linearly proportional to Fahrenheit temperature. 華氏
- **LM35** series are precision integrated-circuit temperature sensors whose output voltage is linearly proportional to Celsius temperature. 攝氏
- They require no external calibration since it is **internally calibrated**.
- Their output voltage changes **10mV for each degree** of temperature change.

Table 10.2

Item	Temperature Range	Accuracy	Output
LM34	-50 F to +300 F	+3.0 F	10 mV/F
LM34C	-40 F to +230 F	+3.0 F	10 mV/F
LM35	-55 °C to +150 °C	+1.5 °C	10 mV/°C
LM35C	-40 °C to +110 °C	+1.5 °C	10 mV/°C
LM35D	0 °C to +100 °C	+2.0 °C	10 mV/°C